

19/05/18


(Lee 9.10) State Machines-

- A machine works on different states at a time
- It may give us different outputs at same input & same state

Example:-

Cycle of a state machine would be like:-


- $S$  = States
- $Z$  = Outputs

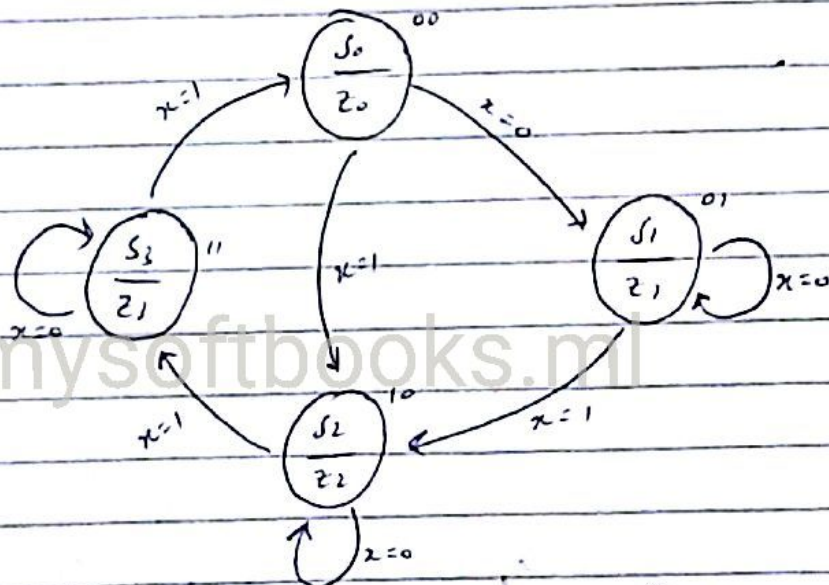

State Tables-

input (x)	Present State	Next State
0	$S_0$	$S_1$
1	$S_0$	$S_2$
0	$S_1$	$S_1$
1	$S_1$	$S_2$
0	$S_2$	$S_2$
1	$S_2$	$S_3$
0	$S_3$	$S_3$
1	$S_3$	$S_0$

Block Diagram:-

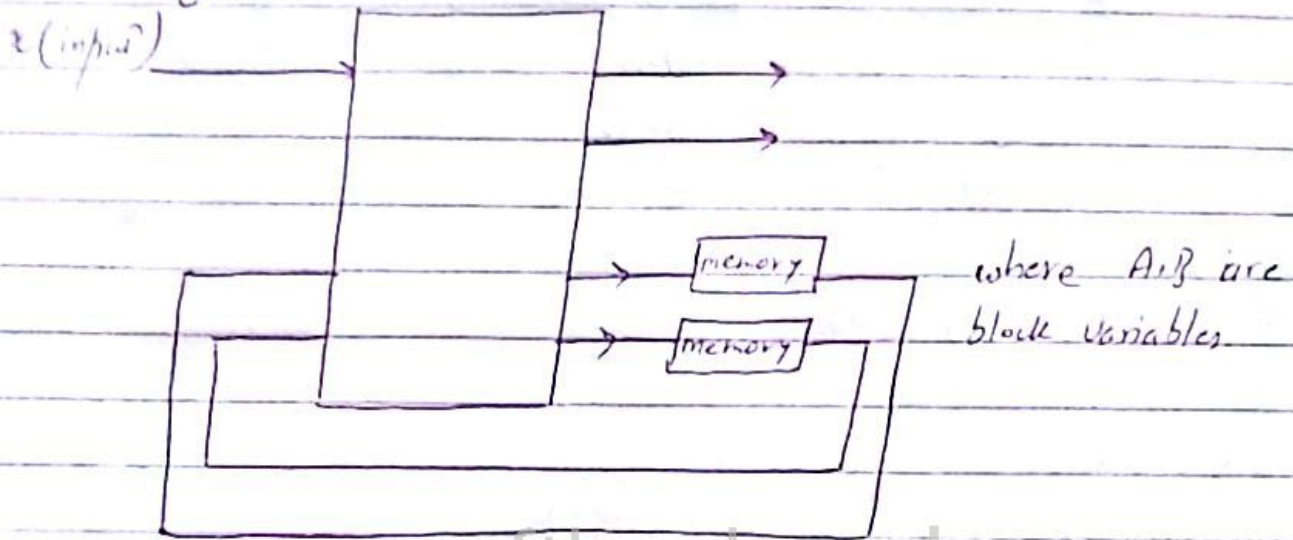


where  $A, B$  are block variables.

mysoftbooks.ml
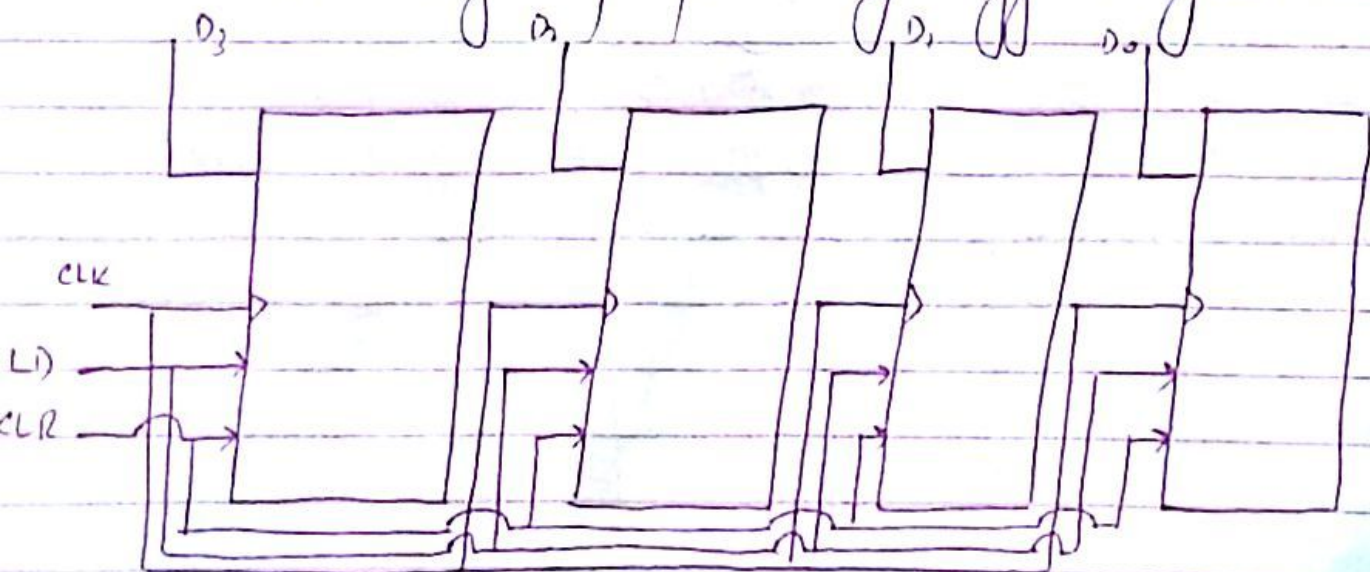
### Registers:-

- They are used to store the data.
- They are edge triggered circuits.

Block Diagram for positive edge triggered Register:-





Inputs in this circuit are-

- i)  $D_0, D_1, D_2, D_3$
- ii) CLK = Clock input to Register
- iii) LD = Load Input
- iv) CLR = To clear the stored data.

- When CLK and LD will be 1 then data will be stored on registers.
- When CLK and CLR will be 1 then data will clear from registers.

Clock (CLK) has two types-

- i) Synchronous Clock (Synchronized)
- ii) A-synchronous Clock (Not-Synchronized)

Types of Regulators:-

There are four types of regulators.

- i)  $V_{in} \rightarrow V_{out}$
  - ii)  $V_{in} \rightarrow P_{out}$
  - iii)  $P_{in} \rightarrow V_{out}$
  - iv)  $P_{in} \rightarrow P_{out}$
- { S = Series }  
{ P = parallel }

## Rules - Block Diagram for Registers -

• For  $S_{in} \rightarrow S_{out}$

Output of one will become input of other. We cannot find out output at middle.

• For  $S_{in} \rightarrow P_{out}$

Output of one will become input of other & we can also check output at any point.

• For  $P_{in} \rightarrow S_{out}$

We can input at any point but output will be checked at the end.

• For  $P_{in} \rightarrow P_{out}$  :-

We can give input at any time & also check output at any point.

## Universal Register -

A register having all four above properties is called Universal Register.




## Counters

- We will use T-Flip flop in counters.

### Up-Counter

- $Q_0$  will start from '0' & will go upward.

### Block Diagram for Up-Counter

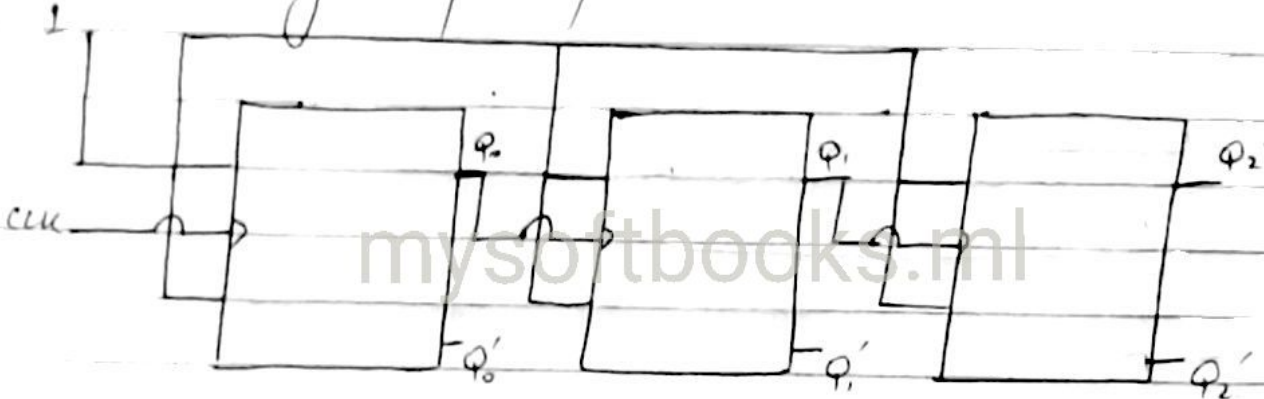

Up-counter is also called Ripple Counter.


### Down-Counter

- In down counters, instead of attaching  $Q$  to the clock of next block, we will attach  $Q'$ .

Two additional inputs used in counters are as follows:-

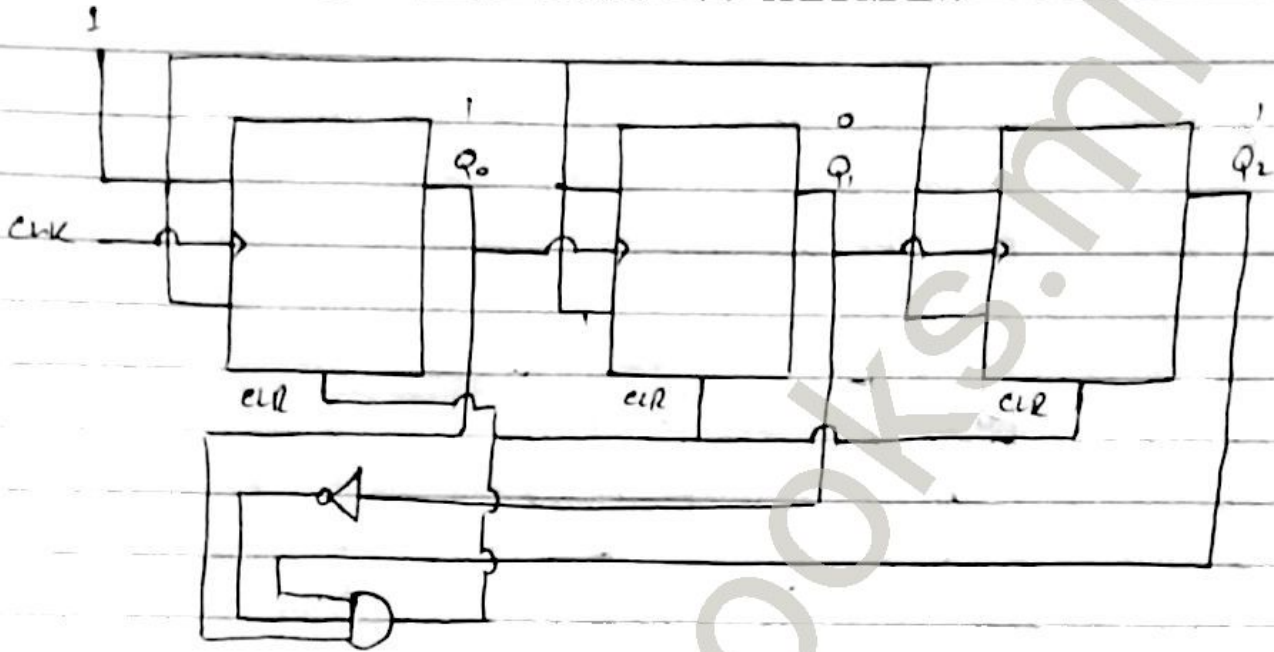- 1)  $PSI$   $\rightarrow$   $Q$  is used to pre-set the value.
- 2)  $CLR$   $\rightarrow$   $Q'$  is used to clear the value.

Block diagram for Counter (Count 0 to 5):



mysoftbooks.com