









Chapter no 2 Logic Gates

(Lecture)
5

Logic Gates and Their Symbols:-

- i) AND Gate 
 - ii) OR Gate 
 - iii) NOT Gate 
 - iv) NAND Gate 
 - v) NOR Gate 
 - vi) XOR Gate 
 - vii) XNOR Gate 
- } universal gate

I_1	I_2	AND	NAND	I_1	I_2	OR	NOR
0	0	0	1	0	0	0	1
0	1	0	1	0	1	1	0
1	0	0	1	1	0	1	0
1	1	1	0	1	1	1	0

XOR 

I_1	I_2	$I_1 \oplus I_2$	$I_1 \odot I_2$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

And \rightarrow "." operator
 OR \rightarrow "+" "
 NOT \rightarrow "~" operator