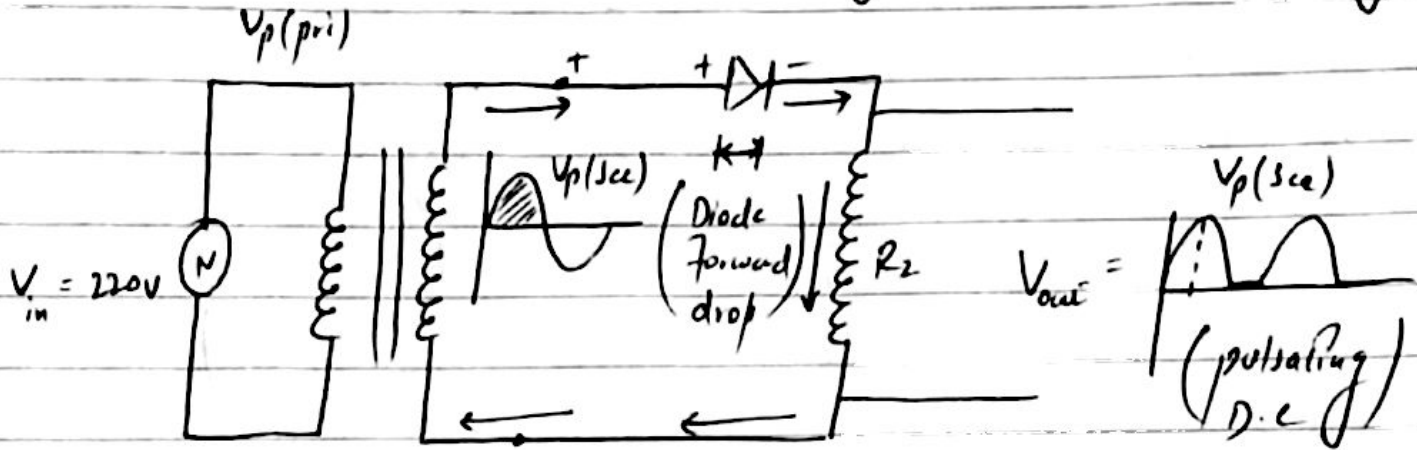


(Lecture
11)

Rectifiers

→ Electronic device or circuit to convert A.C signal into D.C signal.



(Half - Wave Rectifier)

$$V_{(out)} = (V_p(sec) - 0.7V)$$

Factors that affects rectifiers:-

(i) V_{avg} (Average Volt value):-

R_{ms} (Root mean Square Value) = V_{avg}

$$V_{avg} = \frac{1}{2\pi} \int_0^{\pi} V_p(sec) \sin \theta d\theta$$

$$V_{avg} = \frac{V_p(sec)}{2\pi} \int_0^{\pi} \sin \theta d\theta$$

$$V_{avg} = \frac{V_p(\text{sec})}{2\pi} \left(-\cos \theta \Big|_0^{\pi} \right)$$

$$V_{avg} = \frac{V_p(\text{sec})}{2\pi} (\cos \pi - \cos 0)$$

$$V_{avg} = \frac{V_p(\text{sec})}{2\pi} (-1 - 1)$$

$$V_{avg} = \frac{-2 (V_p(\text{sec}))}{2\pi} = \frac{V_p(\text{sec})}{\pi}$$

$$V_{avg} = \frac{V_p(\text{sec})}{3.1415} = \boxed{0.37 V_p(\text{sec})}$$

→ Half-wave rectifier gives us 37% of input in output ($V_p(\text{sec})$).

Limit of Rectifier:-

Peak inverse voltage (PIV) of diode is the broken point.
It should be

$$\boxed{V_{\text{break}} (\text{PIV}) > V_p(\text{sec})}$$